



K16P 1299

Reg. No. : .....

Name : .....

**First Semester M.Sc. Degree (Reg./Suppl./Imp.)  
Examination, November 2016  
(2014 Admission Onwards)  
PHYSICS  
PHY1C04 : Electronics**

Time : 3 Hours

Max. Marks : 60

SECTION – A


Answer **both** questions (Either **a**) or **b**). **Each** question carries **12** marks.

1. a) Draw the basic differential amplifier circuit using transistors and explain. Derive expressions for the AC voltage gain in the single ended and double ended configuration.

OR

- b) Distinguish between combinational sequential logic circuits. Draw the circuit diagram of a master slave JK flip flop and explain its working using a truth table. How is it different from edge triggering ?

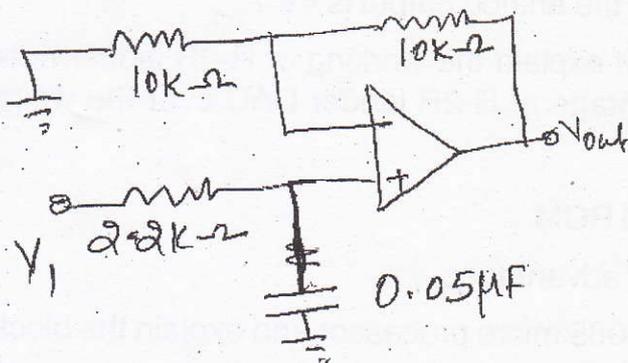2. a) What are active filters ? How are various types of filters classified ? Explain the working of a first order low pass Butter worth filter. Give the frequency response. Calculate the cutoff frequency of a first order low pass filter, given below.



OR

- b) What are the advantages and disadvantages of ripple counters ? Explain the construction and working of a mod-8 ripple counter. What is problem of lock out ? How is it eliminated. (2×12=24)

P.T.O.



## SECTION – B

Answer **any four** questions. **1** mark for Part **a)**, **3** marks for Part **b)**, **5** marks for Part **c)** :

3. a) What is slew rate of an O pamp ?  
b) Obtain the slew rate equation.  
c) Explain the causes and significance of slew rate in applications. How does slew rate differ from transient response ?
4. a) What are waveform generators ?  
b) Explain the construction and working of a triangular wave generator.  
c) Derive the expression for the frequency of oscillation.
5. a) What is a flip flop ? Give its applications.  
b) Distinguish between synchronous and asynchronous latches.  
c) Convert a J-K flip flop into a D- flip flop.
6. a) Explain Universal shift register.  
b) Distinguish between static and dynamic shift registers.  
c) Explain with diagram the working of serial- IN, serial- out shift register. Give the applications of shift registers.
7. a) What is DIA conversion ?  
b) The logic levels used in an 8- bit R-2R ladder DAC are  $0=0V$  and  $1 = 5V$ . What is the binary input when the analog output is  $4V$  ?  
c) With the help of neat diagram explain the working of R-2R ladder network type DAC. What is the advantage of R-2R ladder DAC over the weighted resistor type DAC ?
8. a) Distinguish between RAM and ROM.  
b) What is an EPROM ? Give its advantages.  
c) Draw the functional block of 8085 micro processor and explain the blocks.

(4×9=36)

---